


IX. 1-3

$$P_{\max} = 1600 \text{ VA}$$

$$P_{\min} = -400 \text{ VA}$$

$$Q = ?$$

$$\cos \phi = ?$$

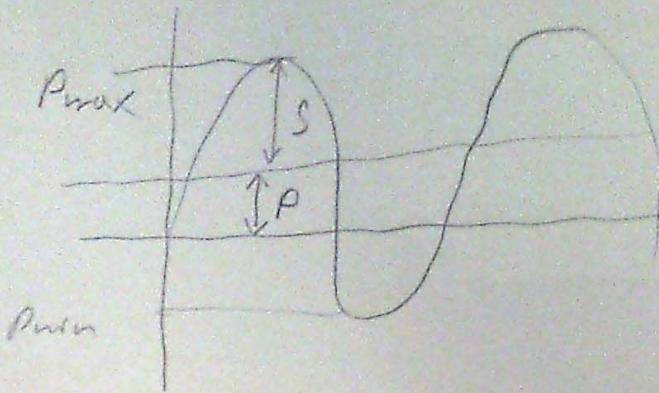

$$P = \frac{P_{\max} + P_{\min}}{2} = \frac{1200}{2} = 600 \text{ W}$$

$$\cos \phi = \frac{P}{S}$$

$$S = 1600 - 600 = 1000 \text{ VA}$$

$$= \frac{600}{1000}$$


$$Q = \sqrt{1000^2 - 600^2} = \boxed{800 \text{ VAr}}$$

$$= \underline{0.6}$$

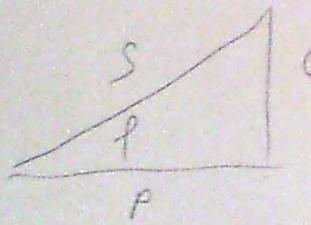IX. 1-4 S se ne zbroja po elementima kao  $Q$  i  $P$ . Rješava se preko trikota slike

$$S_1 = 250 \text{ VA} \quad P_2 = 180 \text{ W} \quad S_3 = 300 \text{ VA}$$

$$\cos \phi_1 = 0.5 \text{ (nd)} \quad \cos \phi_2 = 0.8 \text{ (kap)} \quad Q_3 = 100 \text{ VAr}$$



$$\cos \phi = \frac{P}{S}$$

$$P_3 = \sqrt{300^2 - 100^2}$$

$$= 282.8 \text{ W}$$

$$P_1 = \cos \phi_1 \cdot S_1 = 125 \text{ W}$$

$$P_{\text{uk}} = 125 + 180 + 282.8$$

$$= \boxed{588 \text{ W}}$$

$$Q_1 = \sqrt{250^2 - 125^2} = 216.5 \text{ VAr}$$

$$Q_{\text{uk}} = 216.5 - 135 + 100$$

$$= \boxed{182 \text{ VAr}}$$

$$S_2 = \frac{P_2}{\cos \phi_2} = 225 \text{ VA}$$


$$S_{\text{uk}} = \sqrt{588^2 + 182^2}$$

$$Q_2 = \sqrt{225^2 - 180^2} = 135 \text{ VAr}$$

$$= \boxed{615.52 \text{ VA}}$$

$$= -135 \text{ (jer je cos kap)}$$

IX. 1-3

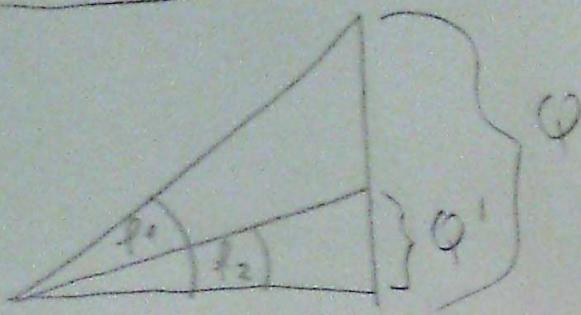

$$Q_R = Q - Q'$$

$$U_n = 220 \text{ V}$$

→ maksimalno opterećenje

$$I_n = 4.5 \text{ A}$$

$$S = U_n \cdot I_n = 990 \text{ VA}$$

$$\cos \varphi_1 = 0.866$$

→ realna snaga i jalova pri  $\varphi_1$

$$\cos \varphi_2 = 0.95$$

$$\cos \varphi_1 = \frac{P}{S} \Rightarrow P = 857.39$$

$$Q = \sqrt{990^2 - 857.39^2} = 495.04 \text{ VAR}$$

→ realna i jalova pri  $\varphi_2$


$$\cos \varphi_2 = \frac{P'}{S} \Rightarrow P' = 990 \cdot 0.95 = 940.5$$

$$Q' = \sqrt{990^2 - 940.5^2} = 309.127 \text{ VAR}$$


$$Q_R = 495.04 - 309.127 = 185.91 \text{ VAR}$$

$$C = \frac{Q_R}{\omega \cdot U^2} = \frac{185.91}{100\pi \cdot 220^2} = \underline{\underline{12.2 \mu F}}$$

IX. 1-5

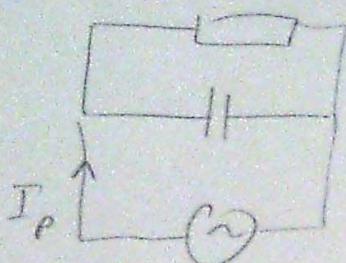

$$\cos \varphi = 0.5$$

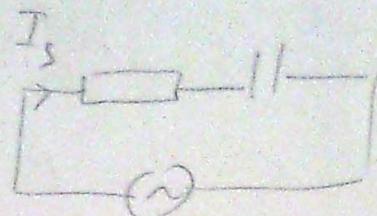

$$\cos \varphi = ?$$

$$Z_p = \frac{R - (-jX_c)}{R - jX_c} \cdot \frac{R + jX_c}{R + jX_c} = \frac{-R^2 X_c + RX_c^2}{R^2 + X_c^2}$$

$$S_p = I_p^2 \cdot Z_p = \left( I_p^2 \cdot \frac{RX_c^2}{R^2 + X_c^2} \right) - I_p^2 \cdot \frac{R^2 X_c}{R^2 + X_c^2} \cdot j = P + Qj$$

$$\cos \varphi = \frac{P}{S}$$

$$\frac{1}{2} = 0.5 = \frac{I_p^2 \cdot \frac{RX_c^2}{R^2 + X_c^2}}{|S_p|} = \frac{I_p^2 \cdot \frac{RX_c^2}{R^2 + X_c^2}}{\sqrt{I_p^4 \cdot \frac{R^2 X_c^4}{(R^2 + X_c^2)^2} + I_p^4 \cdot \frac{R^4 X_c^2}{(R^2 + X_c^2)^2}}}$$

$$\frac{1}{4} = \frac{I_p^4 \cdot \frac{RX_c^2}{(R^2 + X_c^2)^2}}{\frac{I_p^4 R^2 X_c^2 (X_c^2 + R^2)}{(R^2 + X_c^2)^2}} = \frac{\frac{X_c^2}{X_c^2 + R^2}}{\frac{X_c^2 + R^2}{3X_c^2}} \Rightarrow \begin{aligned} X_c^2 + R^2 &= 4X_c^2 \\ 3X_c^2 &= R^2 \end{aligned}$$

$$Z_s = R - jY_c$$

$$S_s = I_s^2, Z_s = I_s^2 \cdot (R - jY_c)$$

$$= (I_s^2 \cdot R) - I_s^2 \cdot Y_c \cdot j = P + Qj$$

$$\cos \varphi' = \frac{P}{|S_s|} = \frac{I_s^2 \cdot R}{\sqrt{I_s^4 \cdot R^2 + I_s^4 \cdot Y_c^2}}$$

$$\cos^2 \varphi' = \frac{I_s^4 \cdot R^2}{I_s^4 (R^2 + Y_c^2)} \Rightarrow \frac{R^2}{Y_c^2 + R^2}$$


Sada vidimo da smo dobili istu izračun  
kao sa  $\cos \varphi$ , samo što u brojniku ima  
 $R^2$  umesto  $Y_c^2$ . Zato obavijemo odnos:

$$3Y_c^2 = R^2 \quad \text{π } \frac{1}{4} \text{ (iz prethodnog izračuna)}$$

$$\cos^2 \varphi' = \frac{3Y_c^2}{Y_c^2 + R^2} = 3 \cdot \frac{1}{4} + \frac{1}{4}$$

$$\cos \varphi' = \frac{\sqrt{3}}{2} = \boxed{0,5 \cdot \sqrt{3}}$$

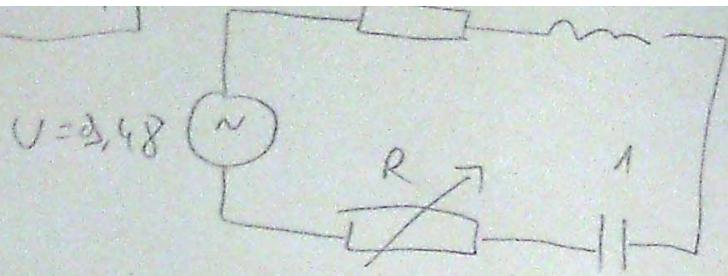NAPOMENA - nisan pisoao molekse oponimo  
i kapacitete i rednim snagama, no  
ocito je da su vrednosti u sekviranju  
i paralelnom spoju



$P_{R\max} = ?$  Ako se samo  $R$  može mijenjati,  
 $R = ?$  tada je (princip IX. 1 - P7)

$$R = \sqrt{R_i^2 + (X_L - X_C)^2} = \sqrt{16 + 9} \\ = \boxed{5 \Omega}$$

$$Z = 4 + 9j + 5 - j = 9 + 3j$$

$$I = \frac{3,48}{9 + 3j} = \frac{237}{250} - \frac{79}{250}j$$

$$P_{R\max} = I^2 \cdot R = \left( \frac{237}{250} - \frac{79}{250}j \right) \cdot 5 = \boxed{9,99 \angle -36^\circ W}$$

IX. 1-8

$$P = 30W \quad U = 220V \quad I = 300mA \quad f = 50Hz$$

$$\rho = U \cdot I \cdot \cos \phi$$

$$\cos \phi = \frac{\rho}{U \cdot I} = \frac{30}{220 \cdot 300 \cdot 10^{-3}} = 0,4545 \Rightarrow \boxed{\phi = 63^\circ}$$

$$S = I^2 \cdot Z = I^2 \cdot (R + j \cdot X_L) = P + Qj$$

$$= \cancel{R \cdot I^2} + X_L \cdot I^2 j \quad \rightarrow U^2 = U_R^2 + U_L^2$$

$$X_L = \sqrt{\frac{220^2 - I^2 \cdot R^2}{I^2}}$$

$$P = R \cdot I^2$$

$$30 = R \cdot (300 \cdot 10^{-3})^2$$


$$R = \boxed{333,3 \Omega}$$

$$X_L = 653,2 \Omega$$

$$X_L = \omega L = 100\pi \cdot L$$

$$L = \frac{653,2}{100\pi} = \boxed{2,09H}$$

[IX - 1 - 9]

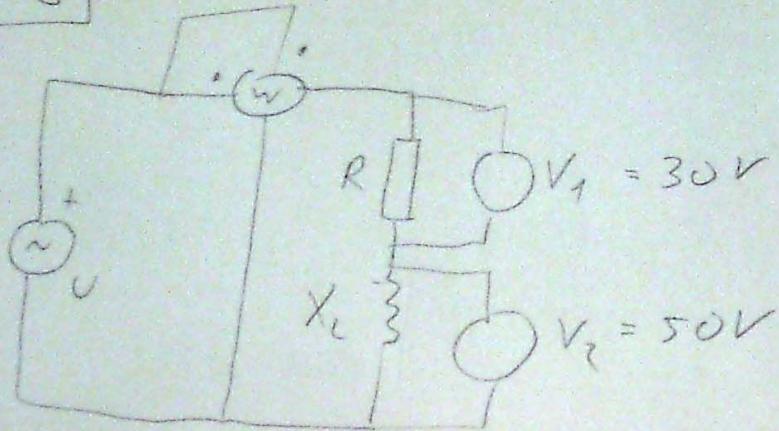

$$P_w = 30 \text{ W}$$

$$U = 30 + 50j \Rightarrow \boxed{58.3 \angle 59^\circ \text{ V}}$$


$$P_w = \frac{U_{V_1}^2}{R} \Rightarrow 30 = \frac{900}{R} \Rightarrow \boxed{R = 30 \Omega}$$

$$I = \frac{U_{V_1}}{R} = \frac{30}{30} = 1 \text{ A}$$

$$P_w = U \cdot I \cdot \cos \varphi$$

$$\cos \varphi = \frac{P_w}{U \cdot I} = \frac{30}{(30+50j) \cdot 1} = \boxed{0.514}$$

[Y - 1 - 10]

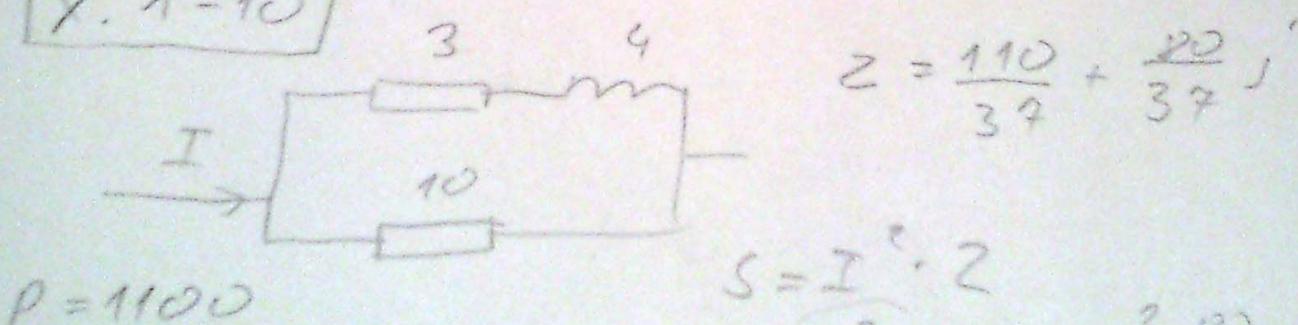

$$Z = \frac{110}{37} + \frac{20}{37} j$$

$$P = 1100$$

$$S = I^2 \cdot 2$$


$$= I^2 \cdot \frac{110}{37} + I^2 \cdot \frac{20}{37} j = P + Qj$$

$$P = I^2 \cdot \frac{110}{37}$$

$$1100 = I^2 \cdot \frac{110}{37}$$

$$\boxed{I = 19.24 \text{ A}}$$

IX. 1-11

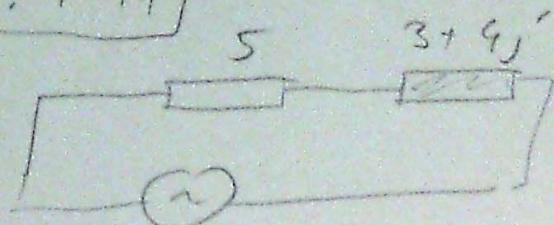

$$Q = 100 \text{ VAr}$$

$$P = ?$$


$$S = I^2 \cdot Z_{th} = I^2 \cdot (5 + 3 + 4j)$$

$$= (8 \cdot I^2) + (4 I^2)j = P + Qj$$

$$P = 8 I^2 \quad Q = 4 I^2$$

$$P = 8 \cdot 5^2 = 200 \text{ W} \quad 100 = 4 I^2 \quad I = 5 \text{ A}$$

IX. 1-12

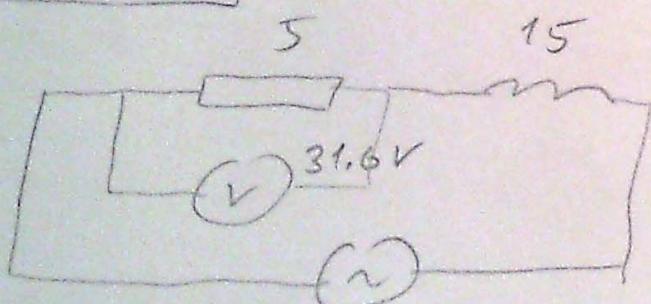

$$S = ?$$


$$S = I^2 \cdot Z$$

$$= 39.992 \cdot (5 + 15j)$$

$$= [199.712 + 599.736j] \text{ VA}$$

$$I = \frac{31.6}{5} = 6.32 \text{ A}$$

IX. 1-13

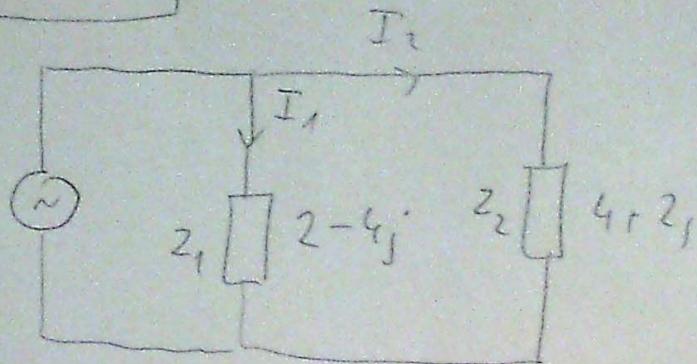

Obje impedancije  
maju istu ef.  
vrijednost otpora  
pa su i stuje  
polnake.

$$I_1 = I_2$$

$$P_{Z_2} = 20 \text{ W}$$

$$P, Q, S = ?$$

$$S_{Z_2} = I_2^2 \cdot Z_2$$

$$= (4 \cdot I_2^2) + [2 \cdot I_2^2] j = P + Qj$$

$$S_{Z_1} = I_1^2 \cdot Z_1$$

$$= 10 + 20j$$

$$P_{Z_1} = 10 \text{ W}$$

$$Q_{Z_1} = -20 \text{ VA}_r$$

$$P_{Z_2} = 4 I_2^2$$

$$20 = 4 I_2^2$$

$$I_2 = \sqrt{5} = I_1$$

$$Q_{Z_2} = 2 \cdot I_2^2$$


$$Q_{Z_2} = 2 \cdot 5 = 10 \text{ VA}$$

$$P_{\text{uk}} = P_{Z_1} + P_{Z_2} = 10 + 20 = 30 \text{ W}$$

$$Q_{\text{uk}} = Q_{Z_1} + Q_{Z_2} = -20 + 10 = -10 \text{ VA}_r = 10 \text{ VA}_r (\text{kao})$$

$$S_{\text{uk}} = \sqrt{P_{\text{uk}}^2 + Q_{\text{uk}}^2} = \sqrt{10000} = 31.6 \text{ VA}$$

S se ne smije zbrojati po elementima, nego  
se dobiva iz rotanta snage

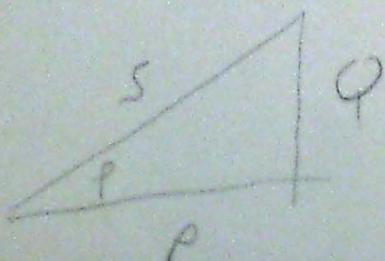

IX. 1-14


$$S_n = 25 \text{ kVA}$$

$$P_T = 12 \text{ kW}$$

$$\cos \varphi = 0.6$$

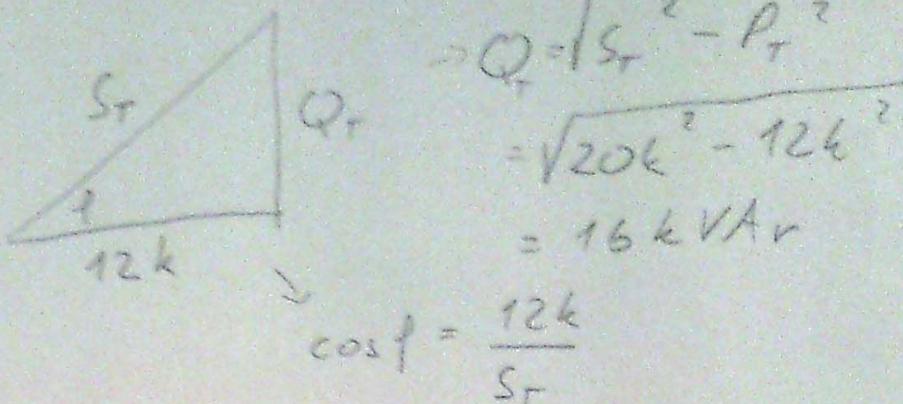a) opterećenost?


$$\frac{S_T}{S_n} = \frac{20k}{25k} = 0.8 = 80\%$$



$$S_T = 20 \text{ kVA}$$

b) Za ovo nisam siguran i ne znam objašnjeno, no rezultat je tu.  
Dodatacna radna snaga do fil opterećenja?

$$P_i = ?$$

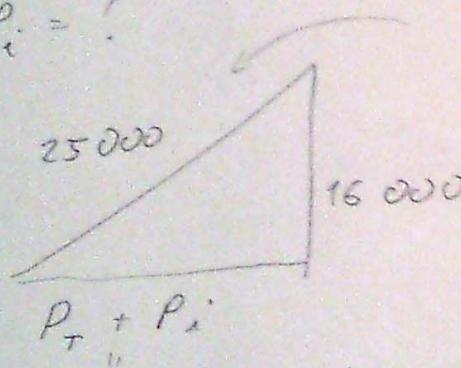

S treba biti 25k kako bi bila ista kao i nazivna

Ne znam zašto Q ostaje isti, vjerojatno zato što ne mijenjamo trojilo

$$25k^2 = (12k + P_i)^2 + 16k^2$$

$$625k^2 = 144k^2 + 24k P_i + P_i^2 + 256k^2$$

$$P_i^2 + 24k P_i - 225k^2 = 0$$


$$P_{i_1} = 4.2 \text{ kW}$$

$$P_{i_2} = -31.8 \text{ kW}$$

Mislim da je  
 $P > 0$

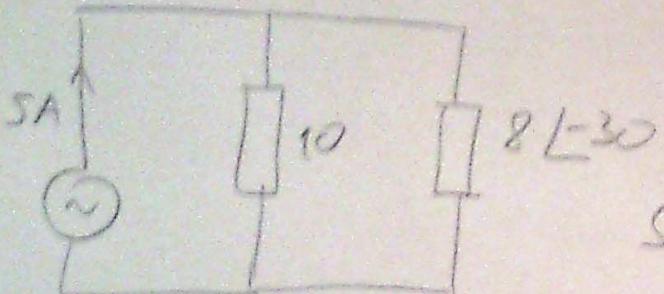IX. 1 - 15

$$Z = 8 \angle -30^\circ = 4\sqrt{3} - 4j$$



$$Z_{th} = 4.40508 - 1.322j$$

$$S = P + Qj = I^2 \cdot Z_{th}$$

$$= (110.127) + 33.0508j$$

$$P = ?$$

$$Q = ?$$

$$P_R = ?$$

$$Q_R = ?$$

$$U = I \cdot Z_{th} = 22.0254 - 6.61j$$

$$P = 110.127 \text{ W}$$


$$Q = -33.058 \text{ VAr} \\ = 33.058 \text{ VAr}$$

(kap.)

$$P_R = \frac{U^2}{R} = 52.88 \angle -33^\circ \text{ W}$$

$$Q_R = \frac{U^2}{8 \angle -30^\circ} = 66.101 \angle -3.4^\circ \text{ VAr}$$

IX. 1-16

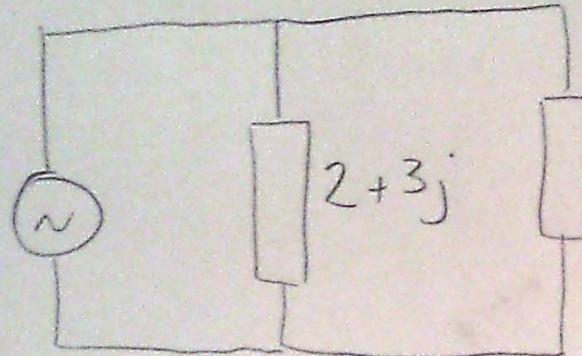

$$Z = \frac{129}{106} + \frac{213}{106} j$$

$$3+6j$$

$$S = P + Qj = I^2 \cdot Z$$

$$= \left( I^2 \cdot \frac{129}{106} \right) + \left( I^2 \cdot \frac{213}{106} \right) j =$$

$$P = 1500 \text{ W}$$

$$Q = ?$$

$$\cos \varphi = ?$$

P

Q


$$1500 = I^2 \cdot \frac{129}{106}$$

$$I = \sqrt{\frac{1500 \cdot 106}{129}} = 35.1098 \text{ A}$$

$$Q = 35.1098^2 \cdot \frac{213}{106}$$



$$= 2476.743 \text{ VAr}$$

$$S = 2895.558 \angle 58.8^\circ$$

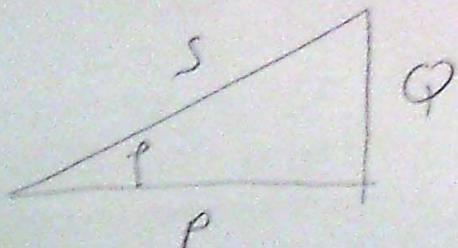

$$\cos \varphi = \frac{P}{S} = \frac{1500}{2895.558} = 0.518$$

IX. 1-17

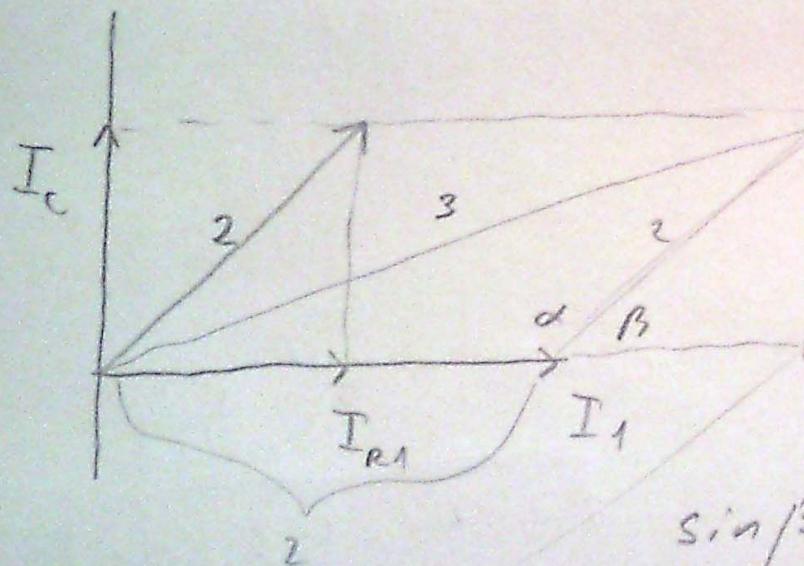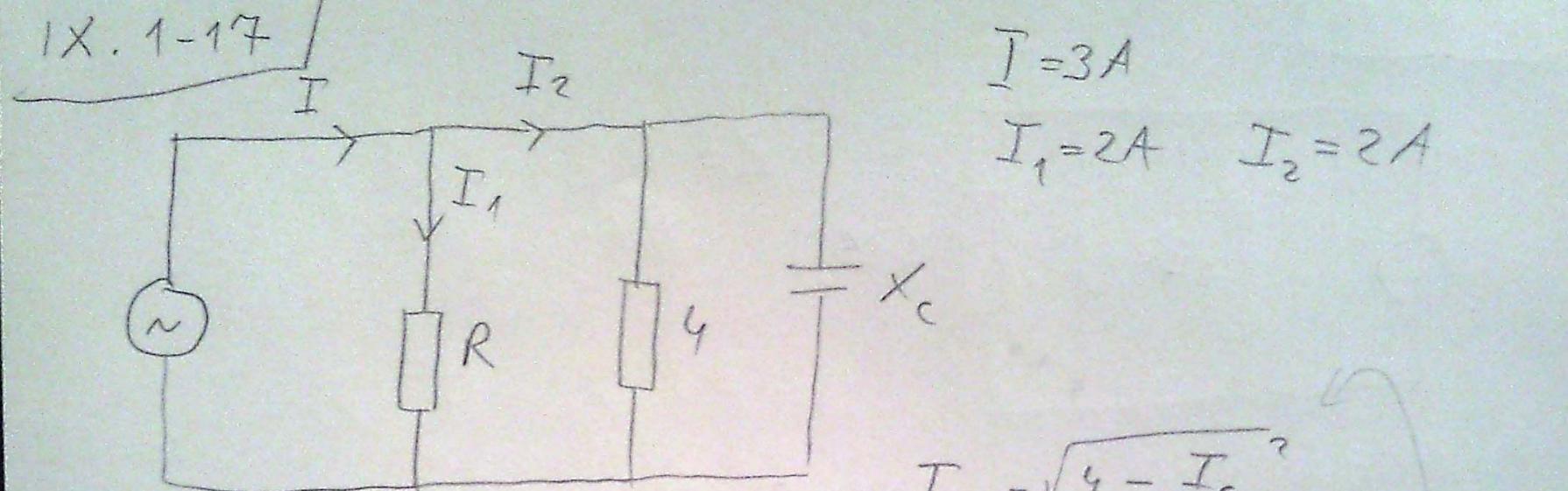

$$I_{R1} = \sqrt{4 - I_c^2}$$

$$= 0,2501 A$$

$$\begin{aligned} g &= 4 + 4 - 8 \cos \alpha \\ \alpha &= 97,18073^\circ \\ \beta &= 82,81925^\circ \end{aligned}$$

$$\sin \beta = \frac{I_c}{2} \quad I_c = 1.9843 A$$

$$U = 0,2501 \cdot 4 = 1.0004 V$$

$$X_C = \frac{U}{I_c} = \frac{1.0004}{1.9843} = 0.50416 \Omega$$

$$Q = \frac{U^2}{X_C} = \frac{1.0004^2}{0.50416}$$

$$= 1.99 VAr$$