

VIII-6 - sličan Pr. 16.

Trošilo sastavljeno od senjskog spoja X_C i R priključeno je na izvor napona U i unutrašnje impedancije \underline{Z}_i . Ako se otpor trošila mijenja u granicama $R_1 - R_2$, pri kojem otporu R će na trošilu biti najveća snaga. Kolika je ta snaga?


$$U = 110 \text{ V}$$

$$\underline{Z} = 4\sqrt{2} \angle 45^\circ \Omega$$

$$X_C = -j10 \Omega$$

$$R_1 = 40 \Omega$$

$$R_2 = 80 \Omega$$

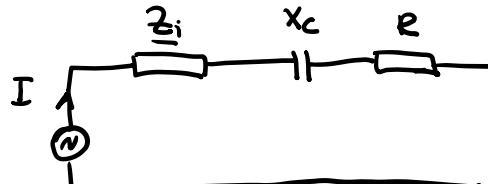

Teorem prijenosa max snage: a) samo R_T ili se samo on mijenja:

$$R_T = \sqrt{R_i^2 + (X_i + X_T)^2}$$

$$= \sqrt{4^2 + (4-10)^2} = 2\sqrt{13} \\ = 7.21 \Omega$$

\nearrow
MAX SNAGE
ZA OVAJ OTPOR

$$R_T = \sqrt{R_i^2 + (X_i + X_T)^2}$$

$$X_T = 0 \rightarrow R_T = \sqrt{R_i^2 + X_i^2 - |Z_i|}$$

b) samo X_T postoji

$$X_T = -X_i$$

c) max. snage trošila

$$\underline{Z}_T = \underline{Z}_i^*$$

Kako to izgleda?

$$i = \frac{U}{\underline{Z}_i + \underline{Z}_T} = \frac{U}{\sqrt{(R_i+R_T)^2 + (X_i+X_T)^2}}$$

$$P_T = I^2 \cdot R_T = \frac{U^2 \cdot R_T}{(R_i+R_T)^2 + (X_i+X_T)^2}$$

Ako uzmemos par vrijednosti R -ova i zapisemo u ovisnosti o U :


$$R = 2 \Omega \rightarrow P_T = \frac{U^2 \cdot 2}{(2+4)^2 + (4-10)^2} = U^2 \cdot 0.0277$$

$$R = 2\sqrt{13} \rightarrow P_T = U^2 \cdot 0.0445986$$

$$R = 40 \rightarrow P_T = U^2 \cdot 0.0202839$$

$$R = 60 \rightarrow P_T = U^2 \cdot 0.0145$$
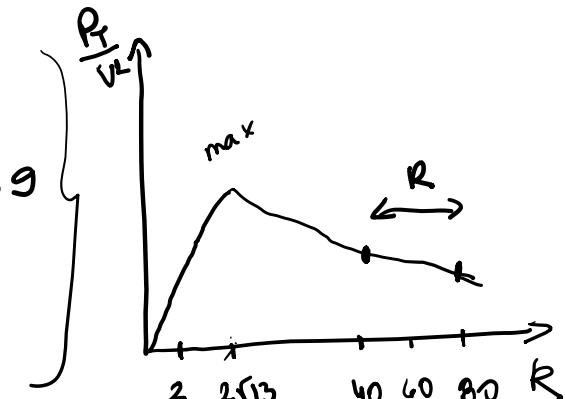
$$R = 80 \rightarrow P_T = U^2 \cdot 0.01128$$



$$R = 40 \Omega$$


$$P = U^2 \cdot 0.0202839$$

$$= 245.435 W //$$

Izvor (transformator) ima nazivnu snagu 25 kVA. Na izvor je priključeno trošilo 12 kW sa faktorom snage 0.6. Odredite:

- postotak opterećenja izvora
 - koliku radnu dodatnu snagu može dati izvor do punog opterećenja?
- Zadatak rješite pomoći trokuta snage.

TROŠILO:

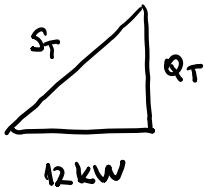

$$P_T = 12 \text{ kW} \quad P_T = S_T \cdot \cos \varphi \rightarrow S_T = \frac{P_T}{\cos \varphi} = 20 \text{ kVA}$$

$$Q_T = \sqrt{S_T^2 - P_T^2} = \sqrt{20^2 - 12^2} = 16 \text{ kVAr}$$

- postotak opterećenja

$$S_n = 25 \text{ kVA} \quad \frac{S_T}{S_n} = \frac{20}{25} = 0.8 \cdot 100\% = 80\%$$

- Ako mijenjamo samo radnu snagu - dakle ne i Q onda:



$$P_T + P_d = 12 \text{ kW} + P_d$$


$$P + P_d = \sqrt{S^2 - Q^2}$$

$$12 \cdot 10^3 + P_d = \sqrt{(25 \cdot 10^3)^2 - (16 \cdot 10^3)^2}$$

$$P_d = 19209.37 - 12000 = 7.209 \text{ kW}$$


VIII-17.

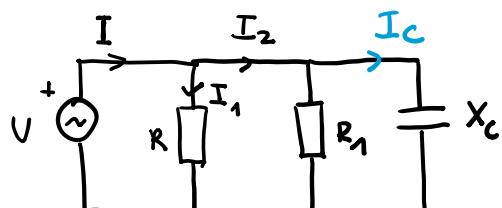Izračunajte reaktivnu snagu u spoju prema sljedećim izmjerenim vrijednostima: $I = 3 \text{ A}$, $I_1 = 2 \text{ A}$, $I_2 = 2 \text{ A}$. Otpornik $R_1 = 4 \Omega$. (X_C nije zadano).



$$Q = \frac{U^2}{X_C} = I_C^2 \cdot X_C$$
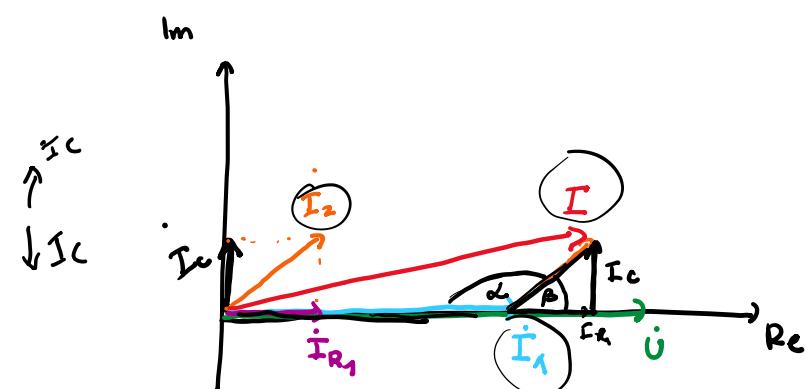
$$X_C = \frac{U}{I_C} \rightarrow \text{trebaju nam i } U \text{ i } I_C$$



$$I_{R1} = \sqrt{I^2 - I_C^2} = \sqrt{4 - I_C^2}$$

KOSINUSOV POUĀAK

$$I^2 = I_1^2 + I_2^2 - 2 \cdot I_1 \cdot I_2 \cdot \cos \lambda$$

$$g = 4 + 4 - 8 \cos \lambda \rightarrow \cos \lambda = -\frac{1}{8} \rightarrow \lambda = 97.18^\circ$$

$$\beta = 180^\circ - \lambda = 82.819^\circ$$

$$\sin \beta = \frac{I_C}{I_2} = \frac{I_C}{2} \Rightarrow I_C = 2 \sin \beta = 1.9843 \text{ A}$$

$$I_{R1} = \sqrt{4 - I_C^2} = 0.2501 \text{ A}$$

$$U = R_1 \cdot I_{R1} = 0.2501 \cdot 4 = 1.0004 \text{ V}$$


$$X_C = \frac{U}{I_C} = 0.50415 \Omega$$

$$Q = \frac{U^2}{X_C} = 1.99 \text{ VAR}$$

$$= I_C^2 \cdot X_C$$


Primer 19 | U tavanju prema slici napon i struja su oblika $U(t) = U_m \sin(\omega t)$, $i(t) = I_m \sin(\omega t)$.

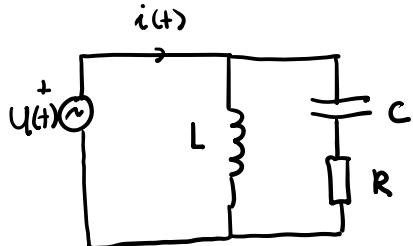Odredite L i C. Zadano: $U_m = 100 \text{ V}$, $I_m = 2.5 \text{ A}$, $\omega = 500 \text{ s}^{-1}$, $R = 20 \Omega$.



$$\dot{U} = \frac{100}{R} \angle 0^\circ \text{ V} \quad X_C = \frac{1}{\omega C} \rightarrow C = \frac{1}{\omega X_C}$$
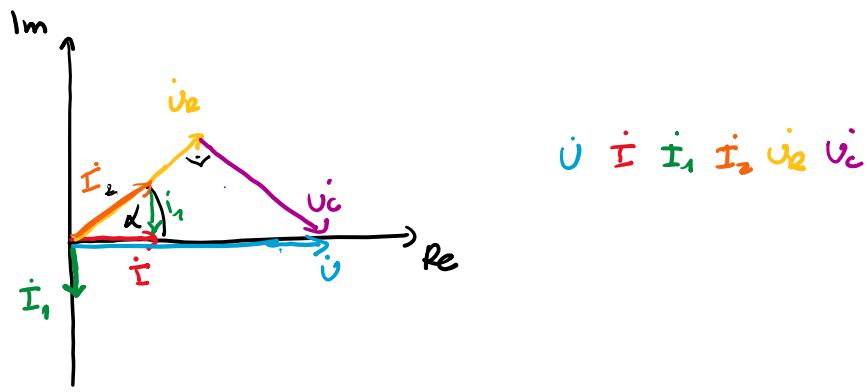
$$\dot{I} = \frac{2.5}{R} \angle 0^\circ \text{ A} \quad X_L = \omega L \rightarrow L = \frac{X_L}{\omega}$$



$$\left. \begin{aligned} \cos \alpha &= \frac{I_2 \cdot R}{U} \\ \cos \alpha &= \frac{1}{I_2} \end{aligned} \right\} \quad \frac{I}{I_2} = \frac{I_2 \cdot R}{U} \rightarrow I_2^2 \cdot R = U \cdot I$$
$$\cos \alpha = \frac{1}{I_2} = \frac{\frac{2.5}{R}}{2.5} = \frac{1}{I_2} \rightarrow \alpha = 45^\circ$$
$$I_2 = \sqrt{\frac{U \cdot I}{R}} = 2.5 \text{ A}$$

$$\dot{U}_R = 2.5 \angle 45^\circ \cdot 20 = 50 \angle 45^\circ = 36.36 + 35.36j \text{ V} \quad \dot{U}_C = \dot{U} - \dot{U}_R$$


$$\dot{U}_C = 35.36 - 35.36j = 50 \angle -45^\circ \text{ V}$$

$$X_C = \frac{U_C}{I_2} = \frac{50 \angle -45^\circ}{2.5 \angle 45^\circ} = 20 \angle -90^\circ \Omega \rightarrow C = \frac{1}{20 \cdot 300} = 100 \mu\text{F}$$

$$I_1 = \sqrt{I^2 - I_2^2} = 1.767 \text{ A}$$

$$\frac{U}{I} = X_L = 40.24 \rightarrow L = 80 \text{ mH}$$

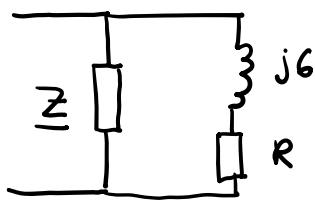Primjer 20. Izračunajte \underline{z} u spoju prema slici ako je snaga na otporniku $R = 3 \Omega$ jednaka $P_R = 666 \text{ W}$. Ukupna prikladna snaga spoja iznosi $S_{uk} = 3370 \text{ VA}$, a faktor snage spoja $\cos \varphi = 0.937$ (kao.)



$$P_{uk} = S_{uk} \cdot \cos \varphi = 3370 \cdot 0.937 = 3157.69 \text{ W}$$

$$P_z = P_{uk} - P_R = 2491.69 \text{ W}$$

$$P_R = I_{RL}^2 \cdot R \rightarrow I_{RL} = \sqrt{\frac{P}{R}} = 14.899 \text{ A}$$

$$\left. \begin{aligned} U_R &= I_{RL} \cdot R = 3 \cdot 14.899 = 44.67 \text{ V} \\ U_L &= I_{RL} \cdot X_L = 8j.394 \text{ V} \end{aligned} \right\} U = \sqrt{U_R^2 + U_L^2} = 99.95 \text{ V}$$

$$\cos \varphi = 0.937 \rightarrow \varphi = 20.446^\circ$$

$$Q_{uk} = S \cdot \sin \varphi = 1177.23 \text{ VAr} \quad (\text{kao})$$

$$Q_L = I_{RL}^2 \cdot X_L = 14.899^2 \cdot 6 = 1332 \text{ VAr}$$

$$Q_z = Q_{uk} - Q_L = -1177.23 - 1332 = -2509.23 \text{ VAr}$$

$$S_z = 2491.69 - 2509.23j$$

$$= \dot{U} \cdot \dot{I}^* = \dot{U} \cdot \dot{U} \cdot \underline{Y}^* = |\dot{U}|^2 \cdot \underline{Y}^* = |\dot{U}|^2 \cdot (G - jB)$$

$$= |\dot{U}|^2 \cdot G - j \cdot |\dot{U}|^2 \cdot B$$

$$|\dot{U}|^2 \cdot G = 2491.69 \rightarrow G = 0.2494 \text{ S}$$

$$|\dot{U}|^2 \cdot B = 2509.23 \rightarrow B = 0.251 \text{ Vs}$$

$$\underline{Y} = 0.2494 + 0.251j \text{ S} \quad \Rightarrow \text{prez. t. slajd 17. predavanje}$$

$$\underline{z} = \underline{Y}^{-1} = 1.99 - 2.00j \quad \Omega$$

1.17. Induktivno trošilo nominalnog napona V_n i nominalne struje I_n povezani su sa mrežnim naponom V i frekvencijom f . Odredite najmanji iznos kapaciteta potrebognog za poboljšanje faktora snage $\cos \varphi$ na iznos $\cos \varphi'$.

$$V = 220 \text{ V}$$

$$V_n = 220 \text{ V}$$

$$I_n = 4.5 \text{ A}$$

$$f = 50 \text{ Hz}$$

$$\cos \varphi = 0.866$$

$$\cos \varphi' = 0.95$$

$$C = ?$$

$$\text{max. opterećenje: } S = I_n \cdot V_n = 990 \text{ VA}$$

$$\text{pri } \varphi: \cos \varphi = \frac{P}{S} \rightarrow P = S \cdot \cos \varphi = 857.34 \text{ W}$$

$$Q = \sqrt{S^2 - P^2} = 495.04 \text{ VAr}$$

$$\text{pri } \varphi'$$

$$\cos \varphi' = \frac{P'}{S'}$$

$$P = P' = 857.34 \text{ W}$$

$$S' = \frac{P'}{\cos \varphi'} = 902.46 \text{ VA} \rightarrow Q' = \sqrt{S'^2 - P'^2} = 281.79 \text{ VAr}$$

$$Q_R = Q - Q' = 495.04 - 281.79 = 213.25 \text{ VAr}$$


C paralelno povezujemo \rightarrow znamo V

$$Q_R = \frac{V^2}{X_C} \rightarrow X_C = \frac{V^2}{Q_R} = 226.96 \Omega$$

$$\frac{1}{\omega C} = X_C \rightarrow C = \frac{1}{\omega X_C} = \frac{1}{2\pi \cdot 50 \cdot 226.96} = 14.024 \mu F$$

Faktor snage otpornika i kondenzatora spojenih paralelno iznosi 0.5. Koliki je ako ih spojimo senjski?

Dakle imamo sljedeće:

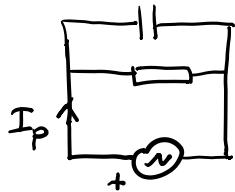

Znamo da je faktor snage $\cos \phi = \frac{P}{S}$

Znamo da $S = |z| \cdot |z|$ i znamo $S = P + jQ$

U ovom slučaju: $S = I_p^2 \cdot |z_p|$

$$z_p = ? \quad z_p = \frac{R \cdot (-jX_C)}{R - jX_C} \cdot \frac{R + jX_C}{R + jX_C} = \frac{R^2(-jX_C) + RX_C^2}{R^2 + X_C^2}$$

$$S_p = I_p^2 \cdot \underbrace{\frac{R \cdot X_C^2}{R^2 + X_C^2}}_P - j \underbrace{\frac{R^2 X_C}{R^2 + X_C^2} \cdot I_p^2}_Q$$

Znamo $\cos \phi_p = 0.5$

$$\cos \phi_p = \frac{P}{S} = \frac{I_p^2 \cdot \frac{R \cdot X_C^2}{R^2 + X_C^2}}{I_p^2 \cdot \sqrt{\left(\frac{R \cdot X_C^2}{R^2 + X_C^2}\right)^2 + \left(\frac{R^2 X_C}{R^2 + X_C^2}\right)^2}}$$

$$0.5 = \frac{\frac{R \cdot X_C^2}{R^2 + X_C^2}}{\sqrt{R^2 X_C^4 + R^4 X_C^2}} = \frac{R \cdot X_C^2}{\sqrt{R^2 X_C^4 + R^4 X_C^2}}$$

$$0.5 \sqrt{R^2 X_C^4 + R^4 X_C^2} = R \cdot X_C^2 \quad |^2$$

$$0.25 R^2 X_C^4 + 0.25 R^4 X_C^2 = R^2 X_C^4 \quad |^2$$

$$0.25 R^2 = 0.75 X_C^2 \quad | : 0.25$$

$$R^2 = 3 X_C^2$$

senjska:

$$z = R - jX_C$$

$$S = |z_s| \cdot |z| = |z_s|^2 \cdot R - j \cdot |z_s|^2 \cdot X_C$$


$$\cos \phi_S = \frac{P}{S} = \frac{|z_s|^2 \cdot R}{|z_s|^2 \cdot \sqrt{R^2 + X_C^2}} \quad |^2$$

$$\begin{aligned} (\cos \phi_S)^2 &= \frac{R^2}{R^2 + X_C^2} \\ &= \frac{3 X_C^2}{4 X_C^2} = \frac{3}{4} \end{aligned}$$

$$\rightarrow \cos \phi_S = \frac{\sqrt{3}}{2} \quad //$$

DODATNO

• primjene P ovise o f

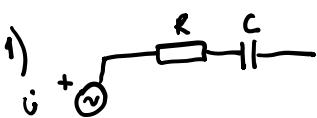

$$x_C = \frac{1}{\omega C} \quad \omega = 2\pi f \\ S = U \cdot I = \frac{U^2}{|Z|} = \frac{U^2}{\sqrt{R^2 + (\frac{1}{\omega C})^2}}$$


$$P = I^2 R = \left(\frac{U}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \right)^2 \cdot R = \frac{U^2 \cdot R}{R^2 + (\frac{1}{\omega C})^2}$$

f v → P v || f ↑ P ↑



$$S = \frac{U^2}{\sqrt{R^2 + (\omega L)^2}} \quad P = I^2 R = \frac{U^2 \cdot R}{R^2 + (\omega L)^2}$$

f ↑ P ↓ || f v P ↑

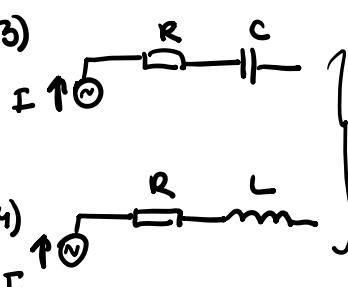


$$P = I^2 \cdot R \rightarrow \text{ostaje isti}$$



$$5) \quad Z_{UK} = \frac{R(-jX_C)}{R-jX_C} \cdot \frac{R+jX_C}{R+jX_C} = \frac{-jR^2X_C}{R^2+X_C^2} + \frac{RX_C^2}{R^2+X_C^2} = \\ = \frac{RX_C^2}{R^2+X_C^2} - j \frac{R^2X_C}{R^2+X_C^2}$$

$$P = I^2 \cdot \operatorname{Re}\{Z_{UK}\} = I^2 \cdot \frac{R \cdot X_C^2}{R^2+X_C^2} = I^2 \cdot \frac{\left(\frac{1}{\omega C}\right)^2 R}{\left(\frac{1}{\omega C}\right)^2 + R^2} = I^2 \cdot \frac{R}{(wC)^2 \cdot R + 1}$$

f v P ↑ || f ↑ P v

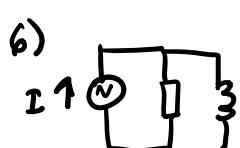


$$Z_{UK} = \frac{X_L^2 R}{R^2+X_L^2} + j \frac{R^2 X_L}{R^2+X_L^2}$$

$$P = I^2 \operatorname{Re}\{Z_{UK}\} = I^2 \cdot \frac{X_L^2 R}{R^2+X_L^2} = I^2 \cdot \frac{R}{\frac{R^2+X_L^2}{X_L^2}} = I^2 \cdot \frac{R}{\frac{R^2}{(wL)^2} + 1}$$


f v P v || f ↑ P ↑

7)

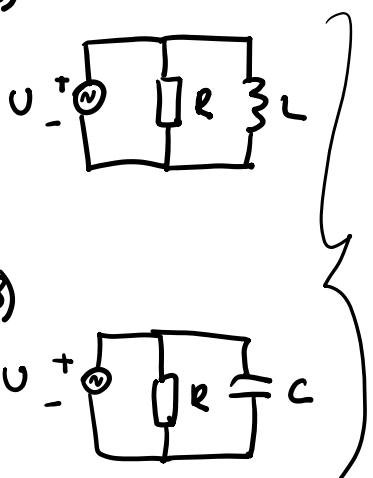


U obo sluzaja R je direktno spojen
na izvor. Dakle snaga se ne mijenja s f.

8)

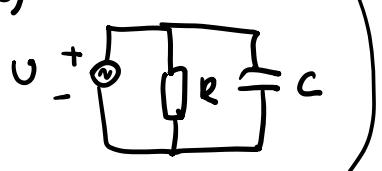


$$P = \frac{U^2}{R}$$

IX.2-1

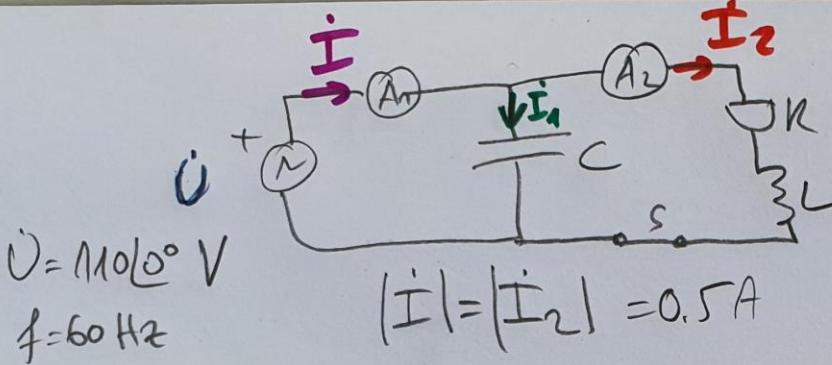

$$I_1 = \frac{U}{jX_C}$$

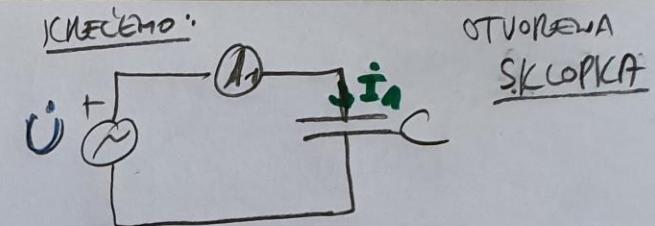





$$|I_1| = 0.5 \text{ A}$$

$$I_1 = \frac{U}{jX_C}$$

$$|I_1| = \frac{U}{X_C}$$

$$X_C = \frac{U}{I_1} = 220 \Omega$$
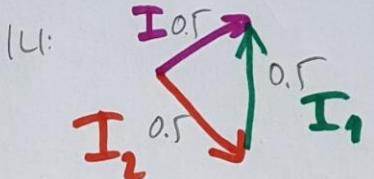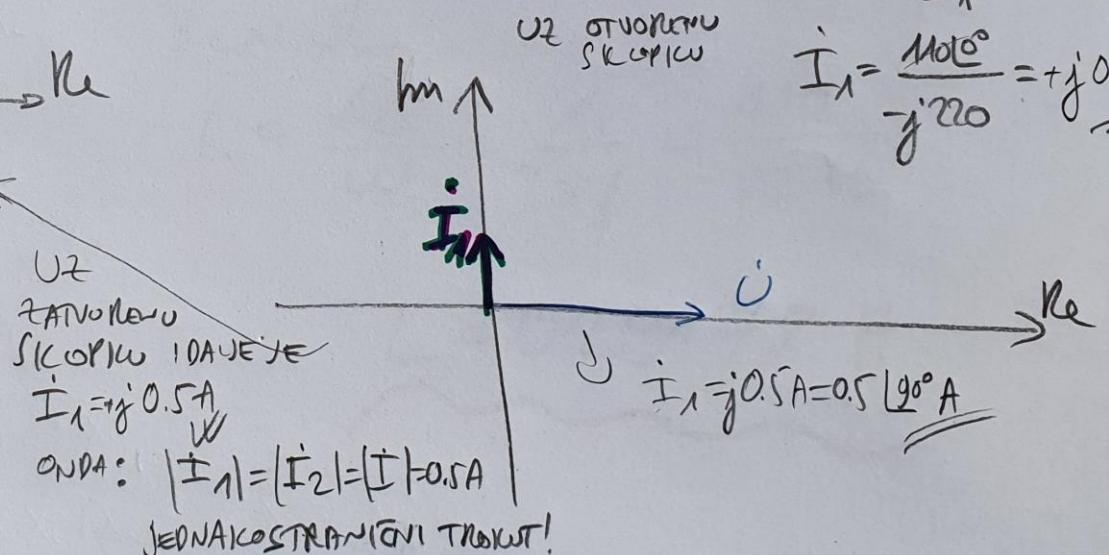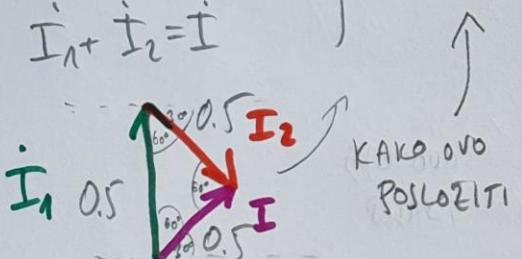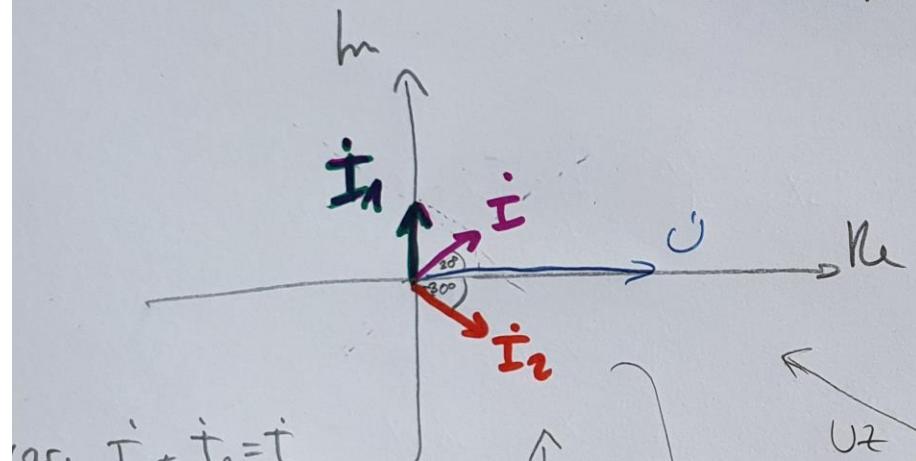
$$I_1 = \frac{110\angle 0^\circ}{j220} = +j0.5 \text{ A}$$



DAKLE ZNAMO:

$$I_2 = 0.5 \angle 30^\circ \text{ A}$$

$$\underline{Z}_{RL} = \frac{U}{I_2} = \frac{110\angle 0^\circ}{0.5 \angle 30^\circ} = 220 \angle -30^\circ \Omega$$

$$\underline{Z}_{RL} = 220 \cdot 0.730 + j220 \cdot \sin 70^\circ$$

$$Z_R = 220 \cdot \frac{\sqrt{3}}{2} + j 220 \cdot \frac{1}{2} = 110\sqrt{3} + j 110 \Omega$$

$\nearrow R$
 $\uparrow X_L$

$$R = 190.526 \Omega$$


$$X_L = 110 \Omega$$

$$X_L = \omega L$$

$$L = \frac{X_L}{\omega} = \frac{X_L}{2\pi f} = \frac{110}{2\pi \cdot 60}$$

$$L = 0.29178 \text{ H}$$

IX.2-3

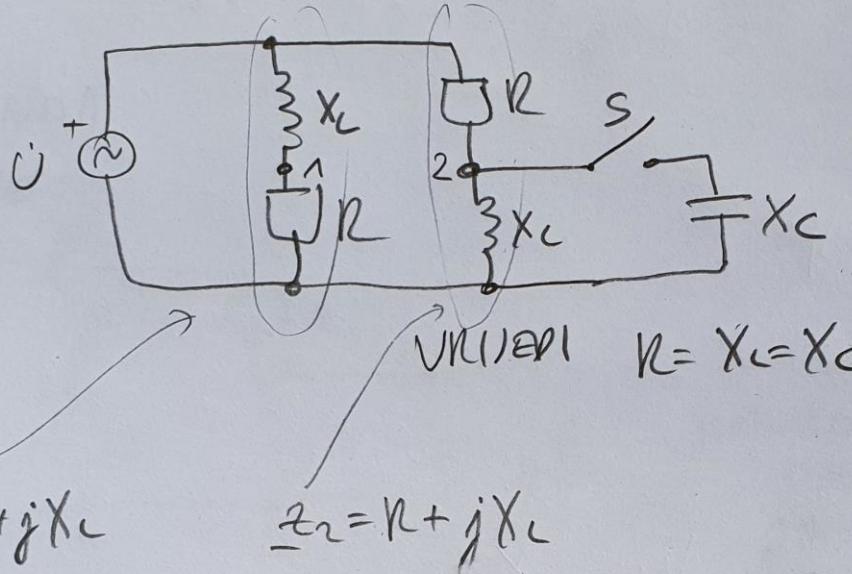


U_{12} uz otvorenim
sklopku

$$U_{12} = 100 \angle 0^\circ V$$

KOJKI JE U_{12}
KADA SE SKLOPKA
ZANORI?

PRIJE ZANARANJA SKLOPKI:

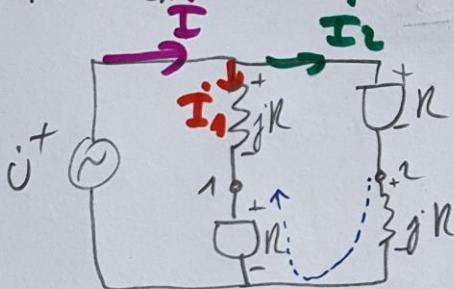

$$U_{12} = 100 \angle 0^\circ$$

PROLAZIMO

KNOT STAVU

OD 2 → 1

AKO ULAZIMO NA + TROSKA / izvora
STAV UANTO —

$$\begin{aligned} \dot{I}_1 &= \frac{\dot{U}}{\underline{Z}_1} = \frac{\dot{U}}{R + jR} \\ \dot{I}_2 &= \frac{\dot{U}}{\underline{Z}_2} = \frac{\dot{U}}{R + jR} \end{aligned}$$

$$\left. \begin{aligned} \dot{I}_1 &= \dot{I}_2 \\ \dot{I} &= \dot{I}_1 + \dot{I}_2 \\ \dot{I} &= 2 \cdot \frac{\dot{U}}{R + jR} \end{aligned} \right\} \text{ISPO! } \dot{I}_1 = \dot{I}_2$$

$$K2S: R \quad \frac{X_L}{2}$$

$$\dot{I} = \dot{I}_1 + \dot{I}_2$$

$$\dot{I} = 2 \cdot \frac{\dot{U}}{R + jR}$$

$$U_{12} = -\dot{I}_2 \cdot jR + \dot{I}_1 \cdot R$$

$$100 \angle 0^\circ = -\frac{\dot{U}}{R + jR} \cdot jR + \frac{\dot{U}}{R + jR} \cdot R$$

$$100 \angle 0^\circ = -\frac{\dot{U}}{R(1+j)} \cdot jR + \frac{\dot{U}}{R(1+j)} \cdot R \quad | \cdot (1+j)$$


$$100 \cdot (1+j) = -j\dot{U} + \dot{U} \Rightarrow \dot{U}(1-j) = 100(1+j)$$

$$\dot{U} = 100 \frac{1+j}{1-j} V$$

$$U = 100 \frac{1+j(1+j)}{1-j} \cdot \frac{j}{1+j} = 100 \frac{(1+j)^2}{2} = 100 \frac{1+2j-1}{2} = 100 \cdot \frac{2j}{2}$$

NAKON ZATVANJA

SKLOPLJE:

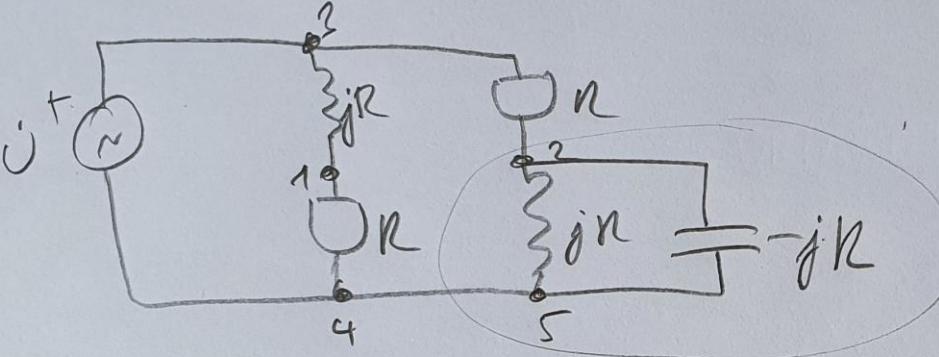


$$\underline{U} = \underline{j}100V$$

KOUKO JE
OVO

$$\frac{jR \cdot (-jR)}{jR - jR} = \frac{R^2}{0} = \infty$$


BESKOMADNI OTROK

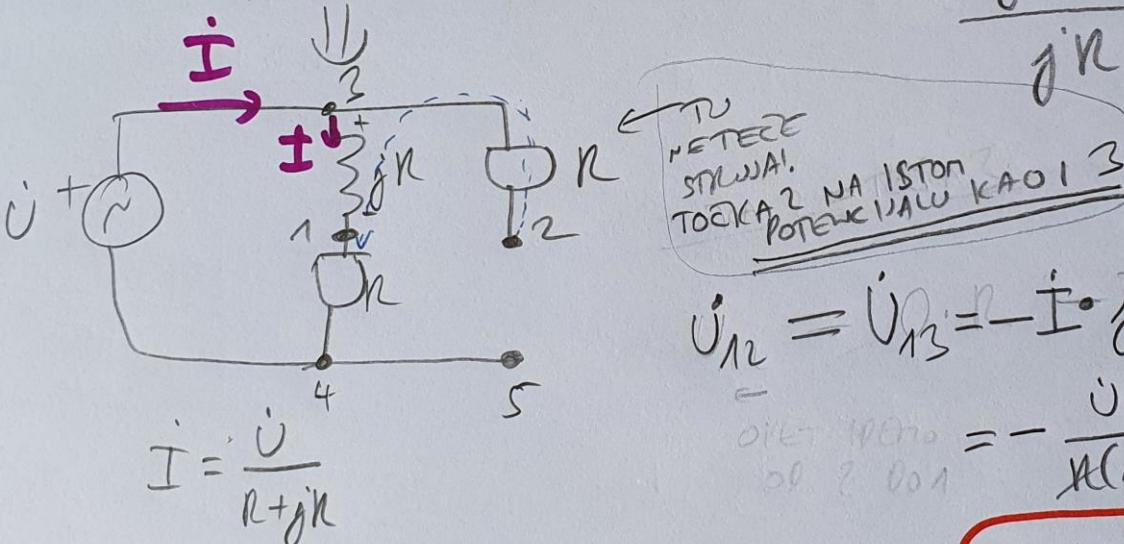

$$U_{12} = U_{13} = -I \cdot jR = -\frac{U}{R+jR} \cdot jR = -\frac{U}{R(1+j)} \cdot jR = -\frac{j100 \cdot j1}{1+j} = \frac{100}{\sqrt{2} \cdot 45^\circ} =$$

$$= \frac{100}{\sqrt{2}} \angle -45^\circ = 70.707 \angle -45^\circ V$$

IX.2-4

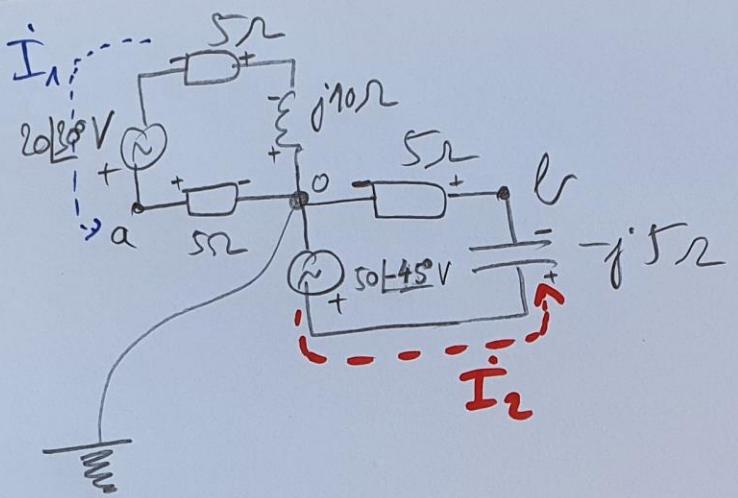

$$I_1 = \frac{20\angle 30^\circ}{5+5+j10} = \frac{20\angle 30^\circ}{10+j10} = \frac{20\angle 30^\circ}{10\sqrt{2}\angle 45^\circ} \Rightarrow$$


$$\underline{I_1 = \sqrt{2} \angle -15^\circ A}$$

$$I_2 = \frac{50\angle 45^\circ}{5-j5} = \frac{50\angle 45^\circ}{5\sqrt{2}\angle 45^\circ} = \frac{10}{\sqrt{2}} \angle 0^\circ A$$

U $\underline{I_2 = 5\sqrt{2} \angle 0^\circ A}$

$$\underline{U_{ab} = }$$

SETNJA
od R do a

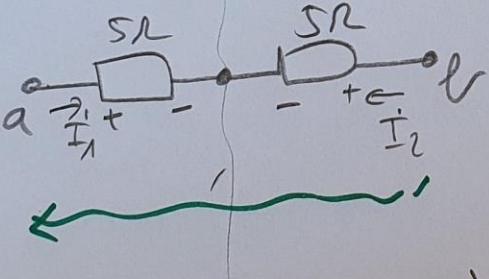


$$\underline{U_{ab} = -I_2 \cdot 5 + I_1 \cdot 5 = -5\sqrt{2} \cdot 5 + 5 \cdot \sqrt{2} \angle -15^\circ = 5\sqrt{2} (5 + 0.9659258263 \angle -0.2588190451)}$$


$$\Rightarrow \underline{U_{ab} = 5\sqrt{2} (-4.034074174 - j 0.2588190451)}$$

$$\underline{|U_{ab}| = 28.5828608 V}$$


IX.2-5

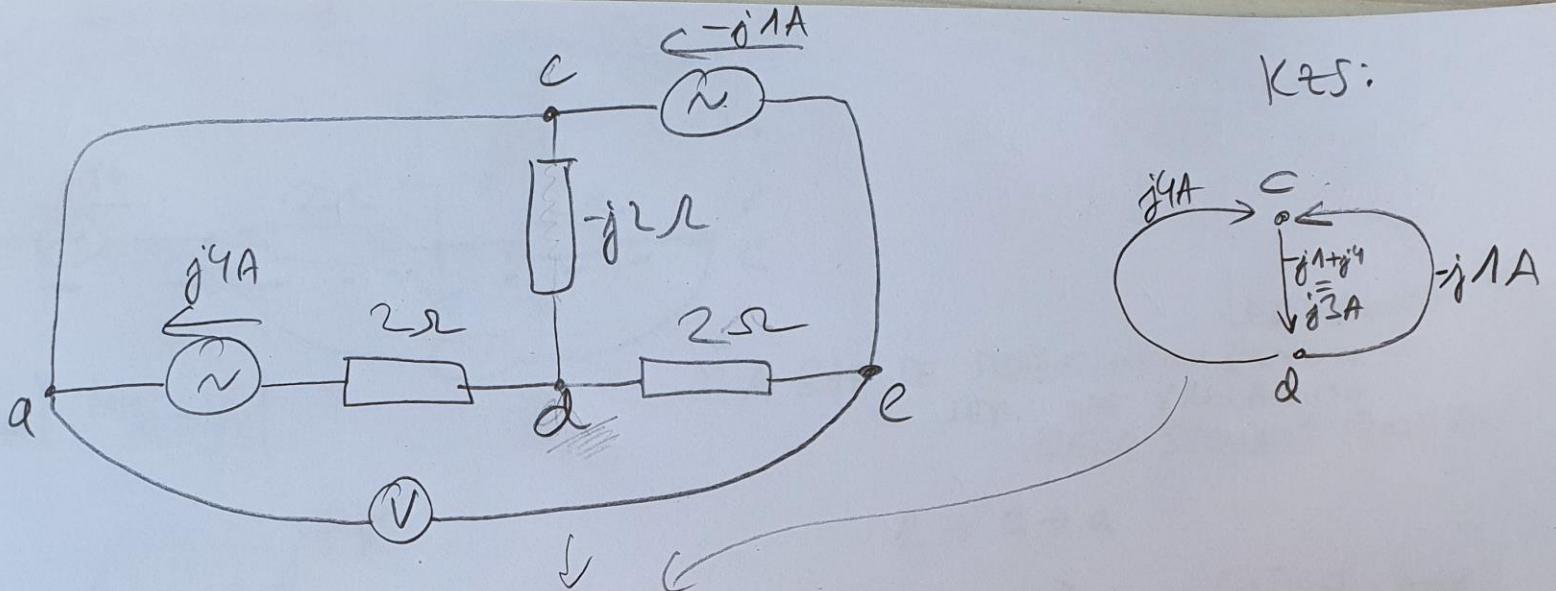

Kz5:

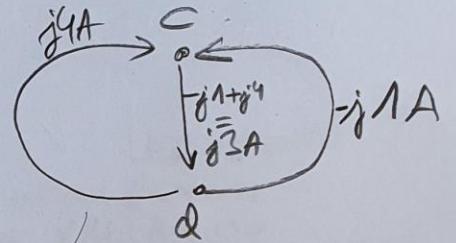

ONDA d ONDA:

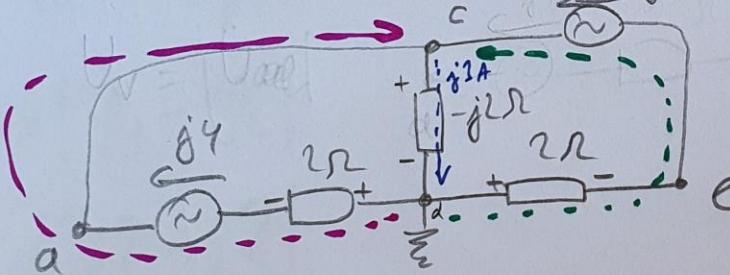

$$j_e = U_{ed} = -(-j1) \cdot 2 = j2 \text{ V}$$

$$j_c = U_{cd} = +(j3A) \cdot (-j2\Omega) = +6 \text{ V}$$


ONDA VI D110:

$$j_a = j_c = +6 \text{ V}$$

$$U_V = |U_{ae}| = |j_a - j_e| =$$

$$= |+6 - j2| = \sqrt{36 + 4} = \sqrt{40}$$

$$U = \sqrt{40} = 2\sqrt{10} \text{ V}$$

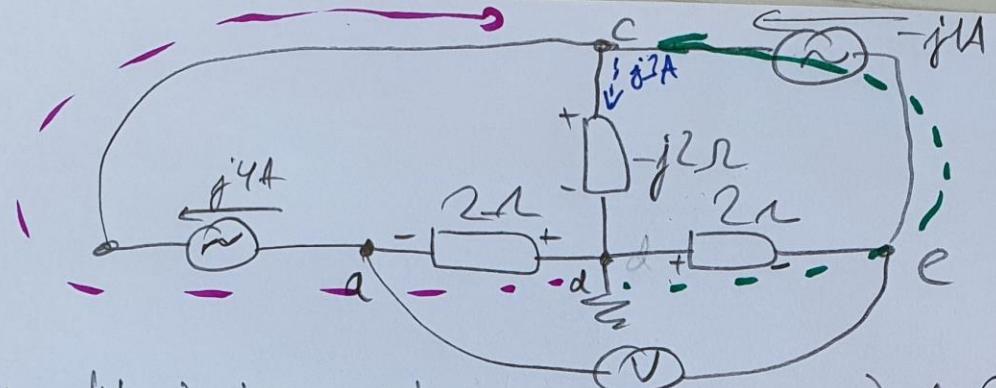

$$U_V = |U_{ae}| = |\dot{\varphi}_a - \dot{\varphi}_e|$$

$$\dot{\varphi}_a = U_{ad} = -j4 \cdot 2 = -j8V$$

$$\dot{\varphi}_e = U_{ed} = -(-j1) \cdot 2 = j2V$$

$$U_V = |\dot{\varphi}_a - \dot{\varphi}_e|$$

$$U_V = |-j8 - j2|$$

$$U_V = |-j10|$$

$$U_V = 10V$$

A SAP SE MOŽEMO ISETATI
JER NE PREDLAŽIMO
PREKO STRUJNOG izvora

e → d → a

$$\begin{aligned} U_{ae} &= +(-j1) \cdot 2 - (j4) \cdot 2 = \\ &= -j2 - j8 = -j10V \end{aligned}$$


ODNOŠTO

$$U_V = |U_{ae}| = 10V$$

(IX.)

10.

TEST PITANJE 10.

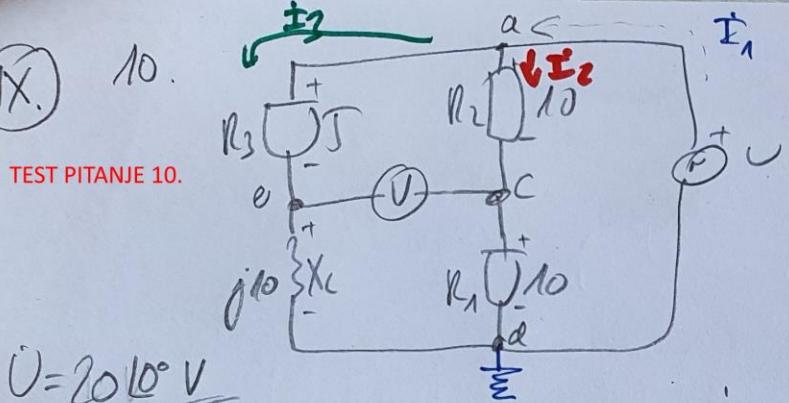




$$\dot{I}_2 = \frac{\dot{U}}{10 + j10} = \frac{\dot{U}}{20} = \frac{20}{20} = 1 \text{ A}$$

$$\dot{U}_c = \dot{U}_{cd} = \dot{I}_2 \cdot 10 = \frac{\dot{U}}{2} = 10 \text{ V}$$

$$\dot{I}_3 = \frac{\dot{U}}{5 + j10} = \frac{20 \angle 10^\circ}{\sqrt{25 + 100} \angle 63.43495^\circ} = \frac{20}{\sqrt{125}} \angle -63.43495^\circ \text{ A}$$

$$\dot{U}_v = \dot{U}_{vd} = \dot{I}_3 \cdot j10 = \frac{200}{\sqrt{125}} \angle 26.56505^\circ \text{ V} = 16 + j8 \text{ V}$$

$$U_v = |\dot{U}_v - \dot{U}_c| = |16 + j8 - 10| = |6 + j8| = \sqrt{36 + 64} = \sqrt{100} = 10 \text{ V}$$

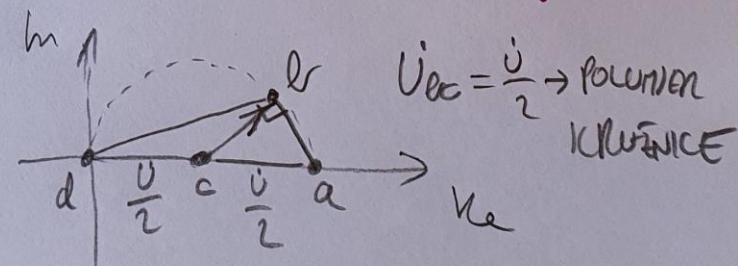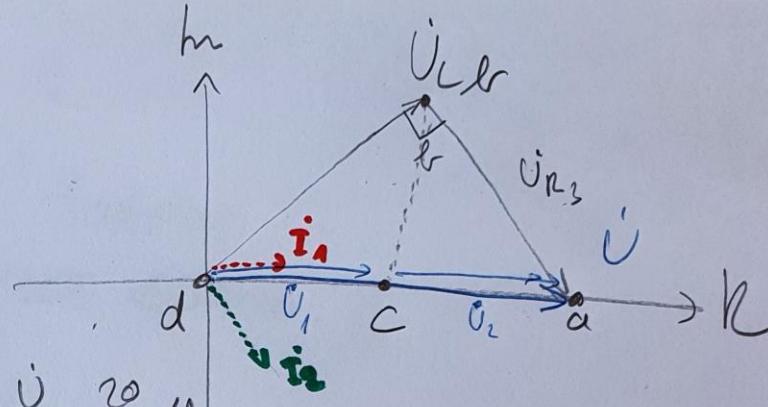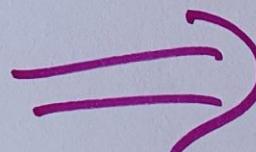


IX, 11.

ONDA IZ GORNJE

iz rješenja: IX - test pitanja 10

IX - test pitanje 11

PRIČE ŽRATO:

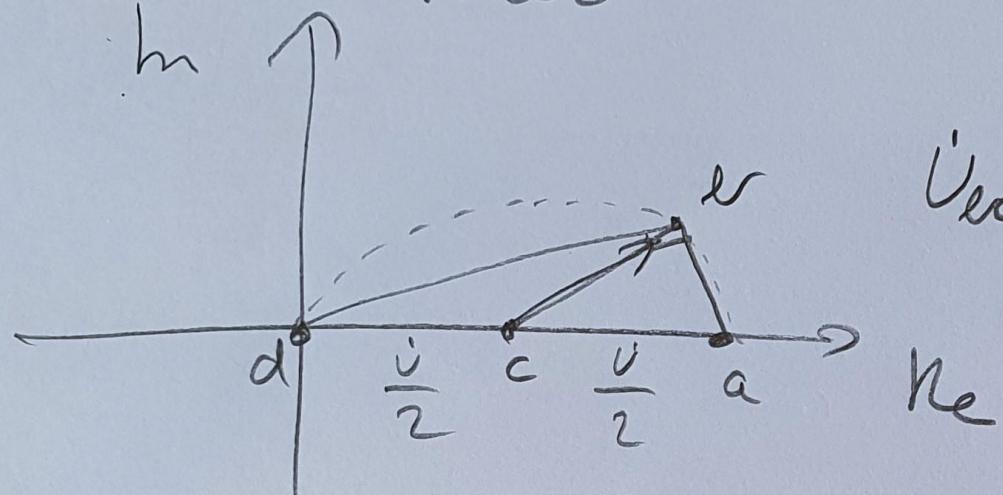

$$U_{ec} = \frac{U}{2}$$

DAKLE

Ako $U_V - |U_{ec}| = 10V$

ONDA

$$\underline{U = 2 \cdot U_V = 20V}$$